



The above is a partial circuit design for an amplifier. The output at A is rated to be 3V when the input is 1mA. α is equal to 5V/mA. Design an interface circuit that will meet these conditions.